

1. A Ge diode has a voltage drop of 0.4 V when 12 mA flows through it. If the same 470 Ohm is used, what battery voltage is needed?

Data:

$$V_D = 0.4 \text{ V}$$

$$I = 12 \text{ mA} = 12 \times 10^{-3}$$

$$R = 470 \Omega$$

$$V_{\text{Battery}} = ?$$

SOLUTION:

P.d across the resistor

$$V_R = I R$$

$$V_R = (12 \times 10^{-3})(470)$$

$$V_R = 5.64 \text{ V}$$

P.d across the battery

$$V_{\text{Battery}} = V_R + V_D$$

$$V_{\text{Battery}} = (5.64) + (0.4)$$

$$V_{\text{Battery}} = 6.04 \text{ V}$$

2. A semiconductor diode laser has a peak emission wavelength of 1.55 μm. Find its band gap in eV.
(0.8 eV)

Data:

$$\lambda = 1.55 \mu \text{ m}$$

$$\lambda = 1.55 \times 10^{-6} \text{ m}$$

$$C = 3 \times 10^8 \text{ m/s}$$

$$h = 6.629 \times 10^{-34} \text{ J s}$$

$$E_{\text{Bandgap}} = ?$$

SOLUTION:

Band gap energy is given by

$$E_B = \frac{h C}{\lambda}$$

$$E_B = \frac{(6.629 \times 10^{-34})(3 \times 10^8)}{(1.55 \times 10^{-6})}$$

$$E_B = \frac{1.9887 \times 10^{-25}}{1.55 \times 10^{-6}}$$

$$E_B = 1.283 \times 10^{-19}$$


Band gap energy in eV

$$1 \text{ eV} = 1.6 \times 10^{-19}$$

$$E_B = \frac{1.283 \times 10^{-19}}{1.6 \times 10^{-19}}$$

$$E_B = 0.801 \text{ eV}$$

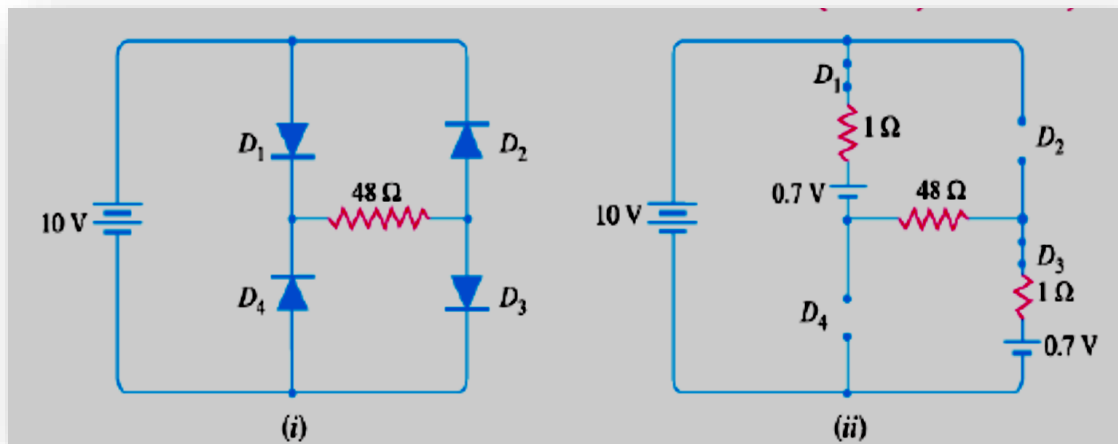3. Calculate the current through $48\ \Omega$ resistor in the circuit shown in Fig. (i). Assume the diodes to be of silicon and the forward resistance of each diode is $1\ \Omega$.



SOLUTION:

For a diode D_1 and D_3 in forward bias and D_2 and D_4 in reverse bias:

The voltage drops across D_1 and D_3 is 0.7 V .

Thus, across D_1 and D_3 combined, the drop is $0.7 + 0.7 = 1.4\text{ V}$.

The total resistance of D_1 and D_3 , due to forward resistance, is $1\ \Omega + 1\ \Omega = 2\ \Omega$

Using Kirchhoff's voltage rule

$$10 - V_{D_1} - V_{48\Omega} - V_{D_3} = 0$$

$$10 - 0.7 - V_{48\Omega} - 0.7 = 0$$

$$10 - 1.4 - V_{48\Omega} = 0$$

$$8.6 - V_{48\Omega} = 0$$

$$V_{48\Omega} = 8.6\text{ V}$$

The total resistance in the circuit includes the series resistance from the diodes
The total resistance is

$$R_{total} = R_{D_1} + R_{48\Omega} + R_{D_3}$$

$$R_{total} = 1 + 48 + 1$$

$$R_{total} = 50\ \Omega$$

We calculate the current I through the circuit


$$I = \frac{V_{48\Omega}}{R_{total}}$$

$$I = \frac{8.6}{50}$$

$$I = 0.172\text{ A}$$

UNIT - 22 SOLID STATE ELECTRONICS

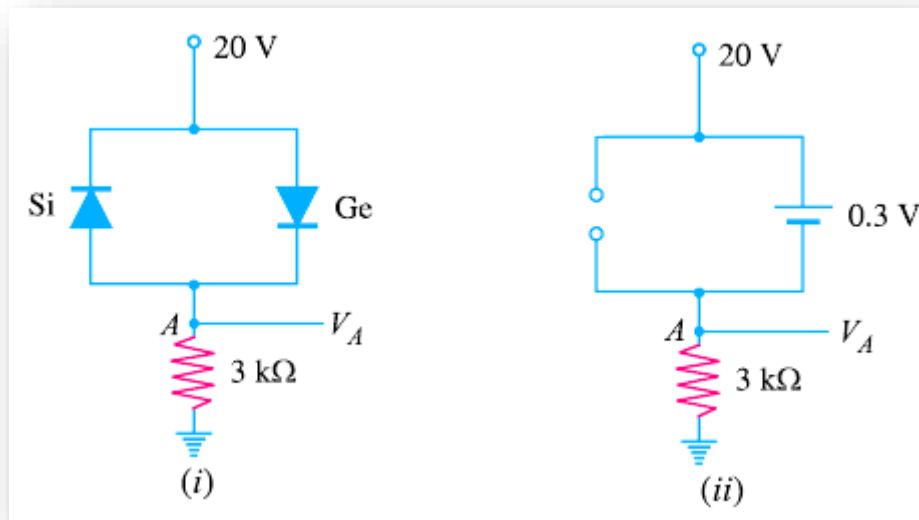4. Find the voltage V_A in the circuit shown in Fig.(i). Use a simplified model.



Data:

The voltage $V_{source} = 20\text{ V}$

Silicon (Si) Diode: reverse voltage drop approximately 0.7 V . when non-conducting

Germanium (Ge) Diode: Forward voltage drop is approximately 0.3 V when conducting.

Using Kirchhoff's voltage rule


$$20 - V_{Ge} - V_A = 0$$

$$20 - 0.3 - V_A = 0$$

$$19.7 - V_A = 0$$

$$V_A = 19.7\text{ V}$$

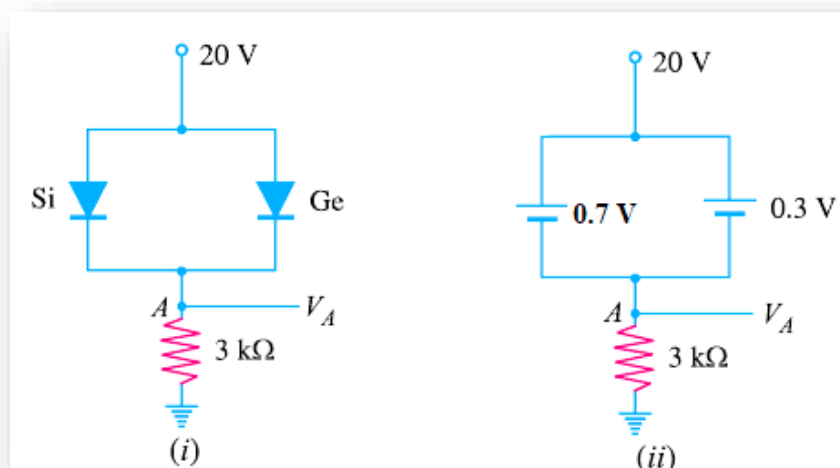- 4(a). Find the voltage V_A in the circuit shown in Fig.(i). Use a simplified model.



Data:

The voltage $V_{source} = 20 \text{ V}$

Silicon (Si) Diode: Forward voltage drop is approximately 0.7 V when conducting.

Germanium (Ge) Diode: Forward voltage drop is approximately 0.3 V when conducting.

Using Kirchhoff's voltage rule

$$20 - V_{Ge} - V_{Ge} - V_A = 0$$

$$20 - 0.3 - 0.7 - V_A = 0$$

$$20 - 1.0 - V_A = 0$$

$$19.0 - V_A = 0$$

$$V_A = 19.0 \text{ V}$$

5. In a common base connection, $I_E = 1 \text{ mA}$, $I_C = 0.95 \text{ mA}$. Calculate the value of I_B .

Data:

$$I_E = 1 \text{ mA} = 1 \times 10^{-3} \text{ A}$$

$$I_C = 0.95 \text{ mA} = 0.95 \times 10^{-3} \text{ A}$$

$$I_B = ?$$

SOLUTIONS

The total emitter current I_E is the sum of the collector current I_C and base current I_B

$$I_E = I_C + I_B$$

$$1 \times 10^{-3} = 0.95 \times 10^{-3} + I_B$$

$$1 \times 10^{-3} - 0.95 \times 10^{-3} = I_B$$

$$0.05 \times 10^{-3} = I_B$$

$$0.05 \text{ mA} = I_B$$

6. Find the value of β if (i) $\alpha = 0.90$ (ii) $\alpha = 0.98$ (iii) $\alpha = 0.99$.

β is given by the following formula:

$$\beta = \frac{\alpha}{1 - \alpha} \dots\dots (i)$$

We can substitute the value of $\alpha = 0.90$

In equation (i)

$$\beta = \frac{0.90}{1 - 0.90}$$

$$\beta = \frac{0.90}{0.10}$$

$$\beta = 9$$

We can substitute the value of $\alpha = 0.98$

In equation (i)

$$\beta = \frac{0.98}{1 - 0.98}$$

$$\beta = \frac{0.98}{0.02} = 49$$

We can substitute the value of $\alpha = 0.99$

In equation (i)

$$\beta = \frac{0.99}{1 - 0.99}$$

$$\beta = \frac{0.98}{0.01} = 98$$

UNIT - 22 SOLID STATE ELECTRONICS

7. Calculate I_E in a transistor for which $\beta = 50$ and $I_B = 20 \mu A$.

DATA

$$\beta = 50$$

$$I_B = 20 \mu A = 20 \times 10^{-6} A$$

$$I_E = ?$$

The collector current I_C is given by:

$$I_C = \beta \times I_B$$

$$I_C = 50 \times 20 \times 10^{-6}$$

$$I_C = 1000 \times 10^{-6} = 1 mA$$

The emitter current I_E is given by:

$$I_E = I_C + I_B$$

$$I_E = 1000 \times 10^{-6} + 20 \times 10^{-6}$$


$$I_E = 1020 \times 10^{-6}$$

$$I_E = 1.020 \times 10^3 \times 10^{-6}$$

$$I_E = 1.020 \times 10^{-3}$$

$$I_E = 1.020 mA$$

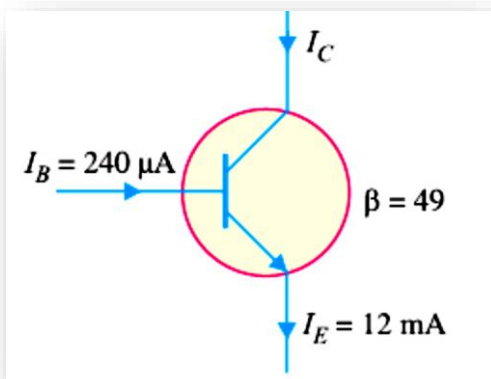8. Find the rating of α The transistor shown in Fig. Hence, determine the value of I_C using both α and the β rating of the transistor.



DATA

$$\beta = 49$$

$$I_B = 240 \mu A = 20 \times 10^{-6} A$$

$$I_E = 12 mA$$

Using the relationship between α and β

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\alpha = \frac{49}{49 + 1}$$

$$\alpha = \frac{49}{50} = 0.98$$

The emitter current I_C is given by:

$$I_C = \beta \times I_B$$

$$I_C = 49 \times 240 \times 10^{-6}$$

$$I_C = 11760 \times 10^{-6}$$

$$I_C = 11.76 \times 10^3 \times 10^{-6}$$

$$I_C = 11.76 \times 10^{-3}$$

$$I_C = 11.76 mA$$