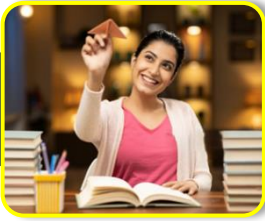


UNIT-23 DIGITAL ELECTRONICS

MULTIPLE CHOICE QUESTIONS

1. The voltage level, typically associated with a 'low' state in digital electronics, is:
(a) -5 volts
(b) **0 volts**
(c) +5 volts
(d) +10 volts
2. In binary representation, the correspondence of '0' in digital electronics is:
(a) **Low state**
(b) High state
(c) Open circuit
(d) Closed circuit
3. The primary purpose of a truth table in digital electronics is to:
(a) Determine input voltage
(b) Measure circuit resistance
(c) **Analyze output states based on input combinations**
(d) Calculate circuit power
4. Which logic gate combination produces an output of '1' when at least one input is '1'?
(a) AND
(b) **OR**
(c) XOR
(d) NOT
5. In a circuit with a 2-input OR gate, the status of the lamp if either switch is closed
(a) OFF
(b) **ON**
(c) Blinking
(d) Flickering
6. The behavior of a 2-input AND gate, when both switches are closed, the Lamp is
(a) OFF
(b) **ON**
(c) blinking
(d) flickering
7. In a 3-input OR gate, if all inputs are '0' so the output will be:
(a) 1
(b) **0**
(c) Undefined
(d) Both A and B
8. If the input is '1', the output of a NOT gate will be:
(a) 1
(b) **0**
(c) Undefined
(d) Both A and B
9. In a 2-input XOR gate, when both inputs are '1', then the output will be
(a) 1
(b) **0**
(c) Undefined
(d) Both A and B
10. Which combination of logic gates is equivalent to an XOR gate?
(a) **AND+ OR**
(b) NOT+ NOR
(c) OR+ NAND
(d) AND+ NAND

UNIT-23 DIGITAL ELECTRONICS



EXAM PRACTICE MCQs

- 1 What are the basic gates in the MOS logic family?
(a) **NAND and NOR**
(b) AND and OR
(c) NAND and OR
(d) AND and NOR
- 2 The universal gate is _____
(a) **NAND gate**
(b) OR gate
(c) AND gate
(d) NOT gate
- 3 The inverter is _____
(a) **NOT gate**
(b) OR gate
(c) AND gate
(d) None of the above
- 4 Identify the logic gate



- (a) AND gate
 - (b) OR gate
 - (c) NAND gate
 - (d) **NOR gate**
- 5 The truth table for a two-input logic gate is as given below

$Y = A \cdot B$		
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Then the logic gate is


- (a) NAND gate
 - (b) **AND gate**
 - (c) OR gate
 - (d) NOR gate
- 6 The truth table for a two-input logic gate is as given below

$Y = A + B$		
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

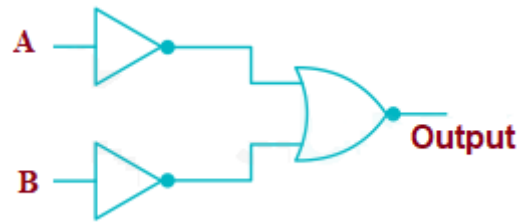- (a) NAND gate
- (b) AND gate
- (c) **OR gate**
- (d) NOR gate

UNIT-23 DIGITAL ELECTRONICS

- 7 Which logic gate is equivalent to these combinations of logic gates



- (a) NOR
(c) **AND**
(b) NAND
(d) OR
- 8 Which one is the Universal Gate?
(a) OR gate
(b) EX-OR gate
(c) **NOR gate**
(d) AND gate

Hint:


A Universal Gate is a gate by which every other gate can be realized.

AND, OR, NOT, etc., are basic gates.

NAND, NOR are the universal gates.

- 9 When both the input signals A and B of the NOR & NAND gate are connected together, The output of the resultant circuit will be equivalent to
(a) OR
(a) **NOT**
(a) AND
(a) None of the above

- 10 Identify the logic gate.

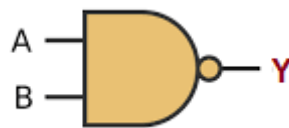

- (a) OR gate
(c) NOT gate
(b) AND gate
(d) **NAND gate**
- 11 The basic gates are:
(a) **AND, NOR, and NOT gates**
(b) AND, OR, and NOT gate
(c) AND and NOT gate
(d) OR and NOT gate
- 12 The logic gating function in DTL is performed by:
(a) **Diode**
(c) Transformer
(b) Inductor
(d) Transistor
- 13 In Boolean algebra, the bar sign (-) indicates _____?
(c) OR operation
(c) **NOT operation**
(c) AND operation
(c) None of the above
- 14 When an input signal 1 is applied to a NOT gate, the output is _____?
(a) **0**
(c) Either 0 & 1
(b) 1
(d) ∞
- 15 If $A = 1$ and $B = 0$, then in terms of Boolean algebra, $A + \bar{B} =$
(a) B
(c) **A**
(b) \bar{A}
(d) 0