

# PHYSICS-XI

## OHM'S LAW, RESISTIVITY, TEMPERATURE CO-EFFICIENT

- 1 A wire carries a current of 1A. How many electrons pass a point in the wire in each second?  
[  $6.25 \times 10^{18}$  electrons ]
- 2 A 40 ohm resistor is to be wound with platinum wire, 0.1 mm in diameter. How much wire is needed ? ( $\rho = 11 \times 10^{-8} \Omega \text{ m}$ )  
[ 2.85 m ]
3. The resistance of a tungsten wire used in the filament of a 60-watt bulb is 240  $\Omega$  when the bulb is hot at a temperature of 2020°C, what would you estimate its resistance at 20°C? (The temperature coefficient of tungsten  $\alpha = 0.0045/^{\circ}\text{C}$ ).  
[ 25.5  $\Omega$  ]
4. Find the resistance at 50 °C of a copper wire 2 mm in diameter and 3 m long.  
( $\rho = 1.6 \times 10^{-8} \Omega \text{ m}$  ,  $\alpha = 0.0039 / ^{\circ}\text{C}$ )?  
[ 0.0183  $\Omega$  ]
- 5 A car headlight filament is made of tungsten and has a cold resistance of 0.350  $\Omega$ . If the filament is a cylinder 4.00 cm long (it may be coiled to save space), what is its radius?. ( $\rho = 5.6 \times 10^{-8} \Omega \text{ m}$ )  
[  $r = 3.2 \times 10^{-9} \text{ m}$  ]

## INTERNAL RESISTANCE OF BATTERY

- 1 A 9 V battery is connected in series with a load and the terminal voltage is found to be 8 V. Current through the circuit is measured as 5 A. What is the internal resistance of the battery?  
[ 0.2  $\Omega$  ]
- 2 A battery has an internal resistance of 0.5  $\Omega$  and an EMF of 1.5 V. When connected in series to a load resistance, the terminal voltage falls to 1.45 V. What current is flowing in the circuit, and what is the value of the load resistance?  
[ 0.1 A, 14.5  $\Omega$  ]
- 3 When no current runs through the circuit, the potential difference across the cell is 3 V. The terminal potential difference lowers to 2.8 Volts while current  $I = 0.37$  Ampere is flowing. What is the cell's internal resistance ( $r$ )? [ 0.54  $\Omega$  ]
- 4 A battery of 24V is connected to a 10 $\Omega$  load and current of 2.2 amp is drawn; find the internal resistance of the battery and its terminal voltage. [ 0.9  $\Omega$  , 22 V ]




## ELECTRICAL POWER AND ENERGY

- 1 A DC winch motor is rated at 20 A with a voltage of 220 V. When the motor is running at its maximum power, it can lift an object with a weight of 4900 N a distance of 20 m, in 40 s, at a constant speed. (a) What is the power consumed by the motor? (b) What is the power used in lifting the object?  
[ 4400 W , 2450 W ]
- 2 A lamp draws a current of 0.20 A when it is connected to a 240 V source. A lamp is used for 30 minutes. How much energy does it require? [  $8.64 \times 10^4 \text{ J}$  ]
- 3 The energy used by the iron for 1 minute is 33 kJ, at a voltage of 220 volts. How large the current is in the iron.  
[ 2.5 A ]

# PHYSICS-XI
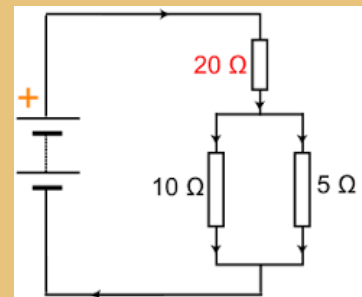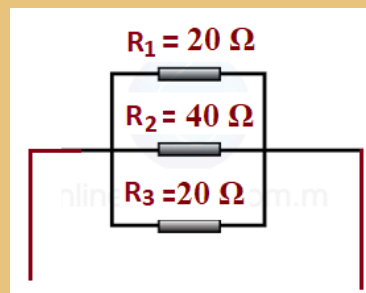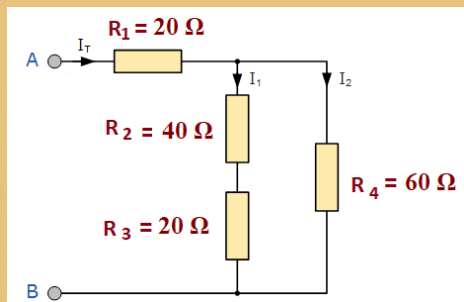
## SERIES AND PARALLEL CIRCUIT





- You are given three resistors each of 2 ohm. How would you arrange these resistors to obtain the equivalent resistances of  
i) 1.5 ohm ii) 3 ohms iii) 6 ohm?  
Also prove the result mathematically.
- Find the equivalent resistance of the circuit.



- A battery with a terminal voltage of 9 V is connected to a circuit consisting of 7Ω, 12 Ω and 8 Ω resistors all in series. Assume the battery has negligible internal resistance. Calculate the  
(i) Equivalent resistance (ii) Calculate the potential drop across each resistor
- Three resistors  $R_1=8\ \Omega$ ,  $R_2=4\ \Omega$ ,  $R_3=12\ \Omega$  are connected in parallel. The parallel connection is attached to a  $V=3.00\text{V}$  voltage source.  
(i) What is the equivalent resistance?  
(ii) Find the current supplied by the source to the parallel circuit
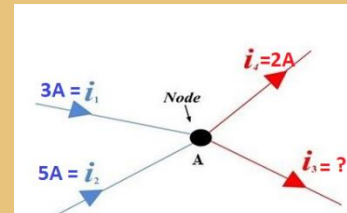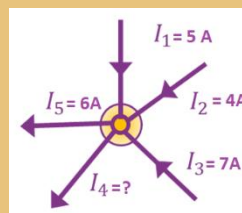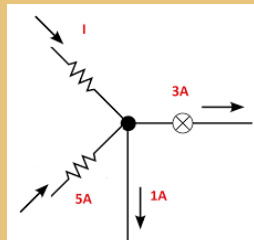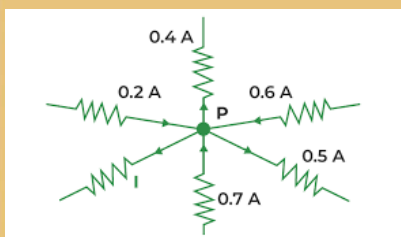
## POTENTIOMETER AND KIRCHHOFF'S LAW

- A potentiometer arrangement, a cell of emf 1.1 volt gives a balance point at 55 cm length of the wire. If a cell is replaced by another cell of emf E, the balance point is obtained at 85 cm. What is the value of E?  
[ 1.7 V ]
- Find the value of I



- By KVL rule find the current flowing through resistance

